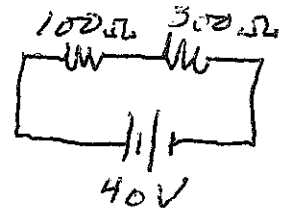


←----- 6 meters -----→

1. What is the wavelength of the wave above? 4 m
2. What is the amplitude of the wave? 0.25 m
3. Assume the frequency of the wave is 2 Hz, calculate the velocity of the wave $v = f\lambda = 8\text{ m/s}$
4. What is the period of the wave? $T = \frac{1}{f} = 0.5\text{ sec}$

5. Given 2 resistors $R_1=100\text{ ohms}$ and $R_2 = 300\text{ ohms}$ connected in series with a battery supplying 40 volts, draw a proper schematic diagram and then calculate the following:


6. Total Resistance of the circuit $400\ \Omega$
7. Total Current through the circuit $I = \frac{V}{R} = 0.1\text{ A}$
8. Voltage across the 100 ohm resistor $V = IR = 10\text{ V}$



9. Describe completely and in detail the method you would use to charge an object by induction. P 510

10. Assuming you have an object outside the focal length of a convex lens, draw a ray diagram and locate and label the image. Indicate if it is real or virtual. P 467

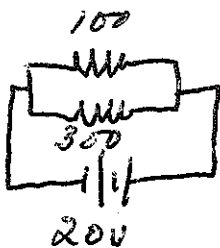11. A 100 ohm resistor and a 300 ohm resistor are connected in parallel to a 20 volt battery. Calculate the total resistance of the circuit and the current through each resistor



$$\frac{1}{R_T} = \frac{1}{100} + \frac{1}{300} = \frac{1}{75} \quad \therefore R_T = 75\ \Omega$$

$$I_{100} = \frac{V_{100}}{R_{100}} = \frac{20\text{ V}}{100\ \Omega} = 0.2\text{ A}$$

$$I_{300} = \frac{V_{300}}{R_{300}} = \frac{20\text{ V}}{300\ \Omega} = 0.0667\text{ A}$$