

Keywords: interface, 5 V, RS-232, ESD, series resistor, current-limiting resistor, protection diode, mixed-voltage signaling, P8X32A

Application Note AN010

Low-cost Bidirectional Mixed-voltage Interfacing

Abstract: The Propeller P8X32A multicore microcontroller's I/O pins feature oversized internal ESD protection diodes. With the appropriate over-current protection, these diodes allow the Propeller to interface with voltage levels above VDD and below VSS.

Introduction

The Propeller P8X32A's I/O pins operate at 0 to V_{DD}, usually 3.3 volts; however, in many cases, a simple resistor may be all that is needed for bidirectional communication between the Propeller chip and a higher voltage device. This application note will focus on choosing the correct current-limiting series resistor value for different voltage levels.

Propeller P8X32A I/O Pin ESD Protection Diodes


Each of the P8X32A's I/O pins contain oversized ESD protection diodes that allow the input to exceed V_{DD}, or fall below V_{SS}, as long as the current sourced or sunk is limited. Using an external current-limiting resistor in series with an I/O pin, a Propeller pin can function as an over-voltage and under-voltage tolerant input. When the I/O pin is operating as an output, this circuitry will have a minimal effect.

When a P8X32A I/O pin is operating as an input and is driven by a signal with a voltage higher than V_{DD} or lower than V_{SS}, the internal ESD protection diodes will clamp to the respective supply rail. The current must not exceed a maximum of 500 µA under the worst-case operating conditions. **ESD protection diode exposure to current over 500 µA may cause damage to the Propeller chip.**

Choosing a Current-limiting Resistor Value

Figure 1 shows a Propeller I/O pin interfaced with an external signal via a series resistor R1.

Figure 1: R1 serves as a current-limiting resistor, providing over-current protection to the Propeller P8X32A's ESD protection diodes

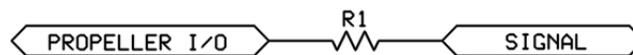

To choose a resistance value for R1, consider the following equation:

$$\text{Minimum Resistance } R1 = \frac{|\text{Signal Maximum } \Delta V|}{\text{Maximum allowed ESD diode current}}$$

The $|\text{Signal Maximum } \Delta V|$ is the largest absolute value of the difference in interface-to-Propeller voltages on the high-side and low-side (positive-to-positive and negative-to-negative). Note that worst-case voltages for both devices must be considered when calculating this value. For the P8X32A the minimum operating voltage is 2.7 V.

The *Maximum allowed ESD diode current* is 500 µA.

Example #1: 5-volt Signal

A 5-volt device may output a signal that transitions from 5 V (high) to 0 V (low). When compared to the Propeller's I/O pin (with a 2.7 V worst-case supply voltage), the high-side absolute Δ voltage is 2.3 V.

$$|5 V_{\text{SIGNAL}}| - |2.7 V_{\text{PROPELLER}}| = 2.3 V$$

The low-side absolute Δ voltage is 0 V.

$$|0 V_{\text{SIGNAL}}| - |0 V_{\text{PROPELLER}}| = 0 V$$

The greater of the absolute values of low-side and high-side is 2.3 V.

$$\begin{aligned} 0 V &? 2.3 V \\ \rightarrow 0 V &< 2.3 V \\ &= 2.3 V \text{ (greatest)} \end{aligned}$$

So the *Minimum Resistance* equation above becomes:

$$\text{Minimum Resistance } R1 = \frac{2.3 V}{500 \mu A}$$

$$2.3 V \div 500 \mu A = 4.6 k\Omega$$

Choose a resistor value for R1 that is at least 4.6 k Ω .

Example #2: RS-232 Device

An RS-232 compliant input must accept voltages from 25 V (high) to -25 V (low). When compared to the Propeller I/O pin's (with a 2.7 worst-case supply voltage), the high-side absolute Δ voltage is 22.3 V.

$$|25 V_{\text{SIGNAL}}| - |2.7 V_{\text{PROPELLER}}| = 22.3 V$$

The low-side absolute Δ voltage is 25 V.

$$|-25 V_{\text{SIGNAL}}| - |0 V_{\text{PROPELLER}}| = 25 V$$

The greater of the absolute values of low-side and high-side is 25 V.

$$\begin{aligned} 25 V &? 22.3 V \\ \rightarrow 25 V &> 22.3 V \\ &= 25 V \text{ (greatest)} \end{aligned}$$

So, the *Minimum Resistance* equation above becomes:

$$\text{Minimum Resistance } R1 = \frac{25 V}{500 \mu A}$$

$$25 V \div 500 \mu A = 50 k\Omega$$

Choose a resistor value for R1 that is at least 50 k Ω .

Revision History

Version 1.0: Original document.

Parallax, Inc., dba Parallax Semiconductor, makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Parallax, Inc., dba Parallax Semiconductor, assume any liability arising out of the application or use of any product, and specifically disclaims any and all liability, including without limitation consequential or incidental damages even if Parallax, Inc., dba Parallax Semiconductor, has been advised of the possibility of such damages. Reproduction of this document in whole or in part is prohibited without the prior written consent of Parallax, Inc., dba Parallax Semiconductor.

Copyright © 2011 Parallax, Inc. dba Parallax Semiconductor. All rights are reserved.

Propeller and Parallax Semiconductor are trademarks of Parallax, Inc. All other trademarks herein are the property of their respective owners.