

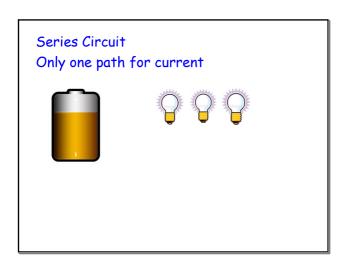



Apr 27-8:36 PM Apr 27-8:46 PM

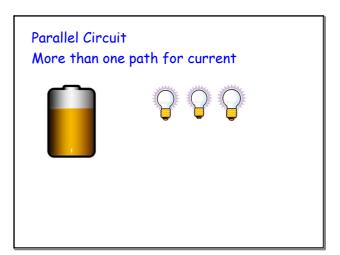

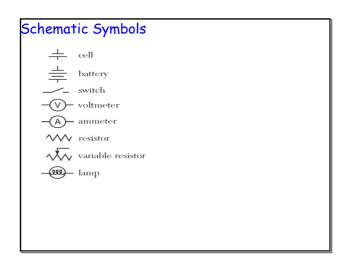

Apr 27-8:50 PM Apr 27-8:50 PM



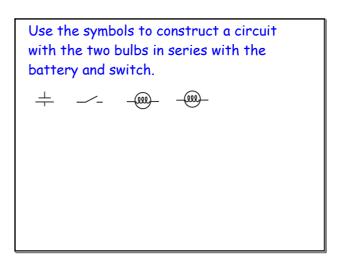

Apr 27-9:02 PM Apr 27-9:19 PM

1

Use the symbols to construct a circuit with the two bulbs in parallel with the battery (no switch).	
<del></del>	